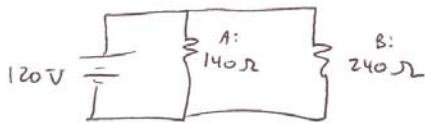


Bulbs rated at 120V, A: 100 watt - $140\ \Omega$ ←
 B: 60 watt - $240\ \Omega$ ←

find resistance of each bulb, since resistance is an unchanging property of each:

$$P = \frac{V^2}{R} \rightarrow R = \frac{V^2}{P} = \frac{(120V)^2}{100W} = \frac{(120V)^2}{60W}$$

(a) Both bulbs get their rated 120V. Circuit looks like this:




start with:

	V	I	R	P
A	120V		140Ω	
B	120V		240Ω	
total	120V			

use ohm's law for A+B; $I = \frac{V}{R}$ and $P = \frac{V^2}{R}$ to get

	V	I	R	P
A	120V	860mA	140Ω	100W
B	120V	500mA	240Ω	60W
total	120V	1360mA	88Ω	160W

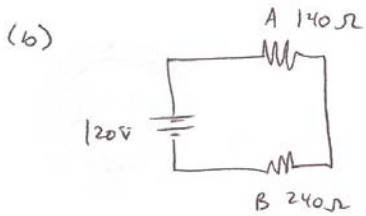

Resistance of each is unchanged;
Power will NOT be as rated!

Series resistors have
380Ω equivalent resistor.

start with:

	V	I	R	P
A			140Ω	
B			240Ω	
total	120V		380Ω	

Solve for total current in the circuit, which is also the current through each bulb; then use ohm's law to fill in.

$$I_{\text{tot}} = \frac{V}{R} = .32 \text{ A} \quad (= 320 \text{ mA})$$

$P = I^2 R$

	V	I	R	P
A	45V	320mA	140Ω	14W
B	77V	320mA	240Ω	25W
total	120V	320mA	380Ω	39W

($V_A + V_B$ don't quite equal 120V because of rounding.)

(c) The brightness of a bulb depends on the power dissipated by the bulb. In part (a), where the bulbs connect to their rated 120V , the bulbs also dissipated their rated power; thus the 100W bulb is brighter.

However, in (b), the bulbs are connected in series, & thus are NOT connected to the 120V they're rated for. The bulbs must split the 120V provided. Since the " 60W " bulb has a bigger resistance, it gets the majority of the 120V from the battery. Since both bulbs get the same current, the " 60W " bulb with more voltage dissipates more power!

Note that even though the " 60W " bulb is brighter than the " 100W " bulb when they're connected in series, both bulbs dissipate less power than they're rated for — thus both bulbs are less bright than when they connect directly to a wall outlet.